 


Q1:

In this question, we should make ALU using the table below and always statement.

Opcode	Function
000	$\text{outW} = 2s\text{Comp}(\text{inA})$
001	$\text{outW} = \text{inA} + 1$
010	$\text{outW} = \text{inA} + \text{inB} + \text{inC}$
011	$\text{outW} = \text{inA} + \text{inB} \times 0.5$
100	$\text{outW} = \text{inA} \& \text{inB}$ (Bitwise)
101	$\text{outW} = \text{inA} \text{inB}$ (Bitwise)
110	$\text{outW} = \{\text{inA}[7:0], \text{inB}[7:0]\}$
111	No operation

First, we draw the circuit:



Part a:


Here is the code:

```
1  `timescale 1ns/1ns
2
3  module Q1_ALU(input signed [15:0] inA, inB,
4               input inC, input [2:0] opc,
5               output reg [15:0] outW,
6               output zero, neg
7           );
8
9
10     always @(inA, inB, inC, opc) begin
11         outW = 16'd0;
12         case (opc)
13             3'b000: outW = ~inA + 1;
14             3'b001: outW = inA + 1;
15             3'b010: outW = inA + inB + inC;
16             3'b011: outW = inA + (inB >>> 1);
17             3'b100: outW = inA & inB;
18             3'b101: outW = inA | inB;
19             3'b110: outW = {inA[7:0], inB[7:0]};
20             3'b111: outW = 16'd0;
21
22             default: outW = 16'bx;
23         endcase
24     end
25     assign neg = outW[15];
26     assign zero = ~|outW;
27
28
29 endmodule
```

Now we have to use testbench to verify our circuit:

```
F:/Madar_CA/CA3/Q1_ALU_TB.v (/tb_ALU) - Default
Ln#
1 `timescale 1ns/1ns
2 module tb_ALU;
3     reg signed [15:0] inpA, inpB;
4     reg inpC;
5     reg [2:0] opcode;
6     wire signed [15:0] outputW, outputWW;
7     wire zero_flag, neg_flag, zero_flag_y, neg_flag_y;
8
9     Q1_ALU uut(inpA,inpB,inpC, opcode,outputW,zero_flag,neg_flag);
10    Q1_ALU_yosys cut(inpA,inpB,inpC,opcode,outputWW,zero_flag_y,neg_flag_y);
11
12    initial begin
13        #100
14        opcode = 3'b000;
15        inpC = 1'b1;
16        inpA = 16'd7;
17        inpB = 16'd64;
18
19        #100 inpC = 1'b0;
20        #100 opcode = 3'b001;
21        #100 opcode = 3'b010;
22        #100 opcode = 3'b011;
23        #100 opcode = 3'b100;
24        #100 opcode = 3'b101;
25        #100 opcode = 3'b110;
26        #100 opcode = 3'b111;
27        #100
28        opcode = 3'b000;
29        inpB = $random;
30        repeat(5) begin
31            #100
32            opcode = $random;
33            inpA = $random;
34        end
35        #100 $stop;
36
37    end
38 endmodule
```

 And this is the timing diagram and the results of it:



Part b:

Now we use Yosys to synthesize the code

(Results of synthesis in Yosys without our library.)

Number of cells is 446.

```
=== Q1_ALU ===  
Number of wires:          436  
Number of wire bits:      483  
Number of public wires:   7  
Number of public wire bits: 54  
Number of memories:       0  
Number of memory bits:    0  
Number of processes:      0  
Number of cells:          446  
$ _AND_                   63  
$ _AOI3_                   48  
$ _AOI4_                    4  
$ _MUX_                    16  
$ _NAND_                   34  
$ _NOR_                    62  
$ _NOT_                    56  
$ _OAI3_                   43  
$ _OAI4_                   14  
$ _OR_                     15  
$ _XNOR_                   72  
$ _XOR_                    19
```

Results of synthesis in Yosys with our library.

```
4.1.2. Re-integrating ABC results.  
ABC RESULTS:      NAND cells:    180  
ABC RESULTS:      NOR cells:     439  
ABC RESULTS:      NOT cells:     137  
ABC RESULTS:      internal signals: 429  
ABC RESULTS:      input signals:   36  
ABC RESULTS:      output signals:  17
```

Number of cells: 756

Part c: There is in the zip file. (the files of pre & post synthesis are called (in order) ->Q1_ALU.v, Q1_ALU_yosys)

Part d:

We made ALU (in first question) by Verilog using software components and elements like 'always', case statement and...so we don't know with which hardware components Verilog implements this circuit.

But in part c, Yosys simulates the hardware by the library provided. And some delays are considered in it. I guess that because part c circuit is completely made with hardware and gates, it is slower than the part one circuit.

Now, we can calculate the times using command "time {run -all}". We should first use "vsim" and then the command above.

Pre synthesis:


```
# Break in Module tb_ALU_2 at F:/Madar_CA/CA3/Q2_ALU_TB.v line 37  
# 207827 microseconds per iteration
```

Post synthesis:

```
# Break in Module tb_ALU_2 at F:/Madar_CA/CA3/Q2_ALU_TB.v line 37  
# 231591 microseconds per iteration
```

Q2:

Here is the hardware of this question:

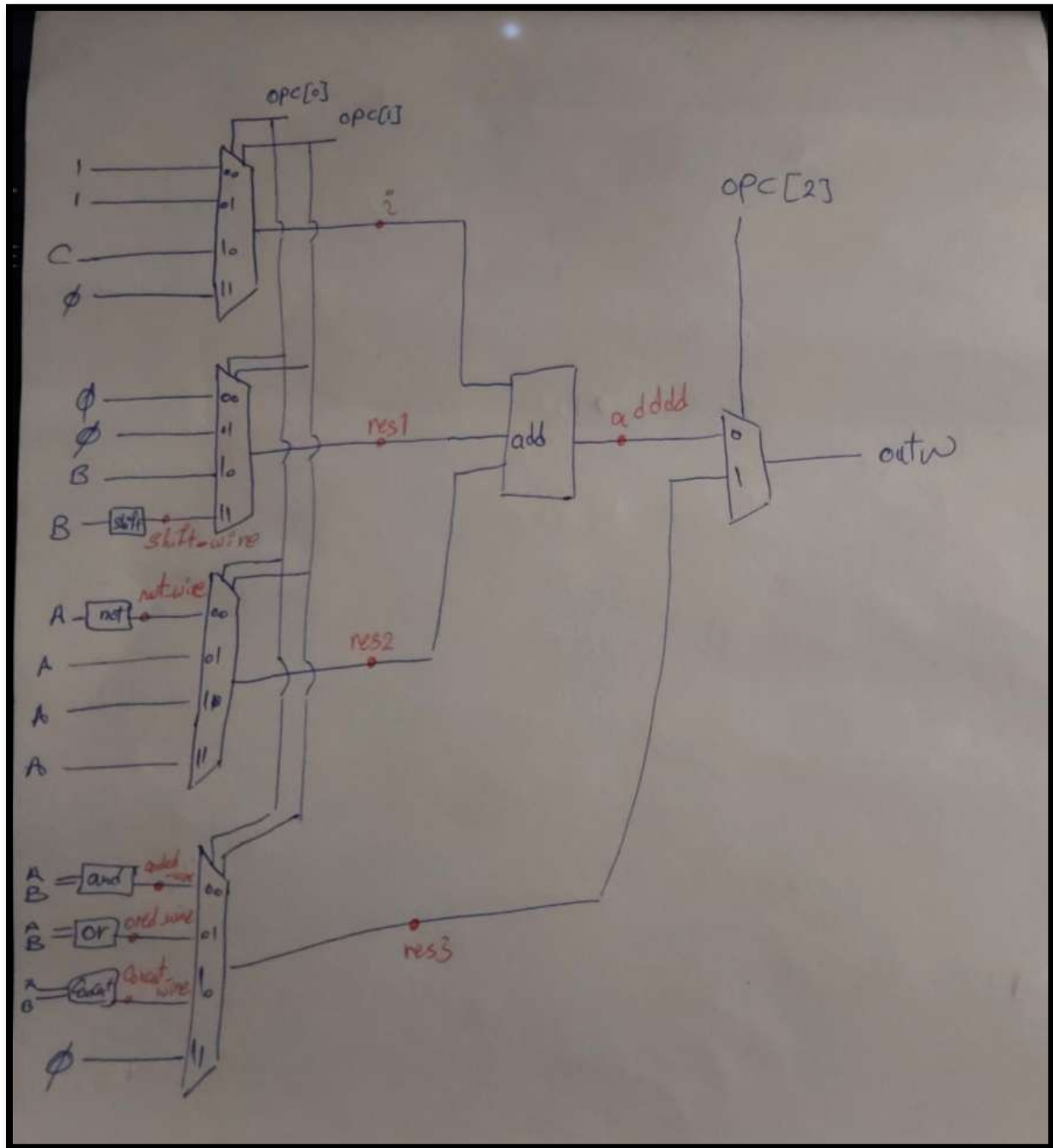


This is the code:

```
1  `timescale 1ns/1ns
2  module mux(output signed[15:0]out,input [1:0]opc,input signed[15:0]a,b,c,d);
3      assign out= (opc==2'b00) ? a:
4                  (opc==2'b01) ? b:
5                  (opc==2'b10) ? c:
6                  (opc==2'b11) ? d:16'b0;
7  endmodule
8
9  module mux_c(output out,input [2:0] opc,input inC);
10     assign out =
11         ((opc[1:0] == 2'b00) || (opc[1:0] == 2'b01)) ? 1'b1:
12         (opc[1:0] == 2'b10) ? inC:
13         (opc[1:0] == 2'b11) ? 1'b0:
14         1'b0;
15 endmodule
16
17 module and_op (output signed[15:0]out,input signed[15:0]a,b);
18     assign out=a&b;
19 endmodule
20
21
22 module or_op (output signed[15:0]out,input signed[15:0]a,b);
23     assign out=a|b;
24 endmodule
25
26 module not_op (output signed[15:0]out,input signed[15:0]a);
27     assign out=~a;
28 endmodule
29
30 module shift_right_op (output signed[15:0]out,input signed[15:0]a);
31     assign out= a>>>1;
32 endmodule
33
34 module adder_op (output signed[15:0]out,input cin,input signed[15:0]a,b);
35     assign out=a+b+cin;
36 endmodule
37
38 module concat_op(output signed[15:0]out,input signed[15:0]a,b);
39     assign out={a[7:0],b[7:0]};
40 endmodule
41
42 module Q2_ALU(input signed [15:0]inA,inB ,input inC,input [2:0] opc
43 ,output reg signed [15:0]outW ,output zer,neg);
44     wire signed[15:0] anded_wire,ored_wire,concat_wire,not_wire,shift_wire,res3,res2,res1,adddd;
45     wire i;
46     and_op and0(anded_wire,inA,inB);
47     or_op or0(ored_wire,inA,inB);
48     concat_op concat0(concat_wire,inA,inB);
49     not_op not0(not_wire,inA);
50     shift_right_op shifter(shift_wire,inB);
51     mux mux1(res3,opc[1:0],anded_wire,ored_wire,concat_wire,16'b0);
52     mux mux2(res2,opc[1:0],not_wire,inA,inA,inA);
53     mux mux3(res1,opc[1:0],16'b0,16'b0,inB,shift_wire);
54     mux_c mux4(i,opc,inC);
55     adder_op adder0(adddd,i,res2,res1);
56     assign outW=(opc[2]==0)?adddd:res3;
57
58     assign neg=outW[15];
59     assign zer= ~|outW;
60
61 endmodule
62
```


This is the test bench for all parts of this assignment:

```
1  `timescale 1ns/1ns
2  module tb_ALU_2();
3      reg signed [15:0] inpA, inpB;
4      reg inpC;
5      reg [2:0] opcode;
6      wire signed [15:0] outputWQ1,outputWQ1Y,outputWQ2,outputWQ2Y;
7      wire zero_flagQ1, neg_flagQ1,zero_flagQ1Y, neg_flagQ1Y,zero_flagQ2, neg_flagQ2,zero_flagQ2Y, neg_flagQ2Y;
8
9
10     Q1_ALU uut(inpA,inpB,inpC, opcode,outputWQ1,zero_flagQ1,neg_flagQ1);
11     Q1_ALU_yosys cut(inpA,inpB,inpC,opcode,outputWQ1Y,zero_flagQ1Y,neg_flagQ1Y);
12     Q2_ALU uuut(inpA,inpB,inpC,opcode,outputWQ2,zero_flagQ2,neg_flagQ2);
13     Q2_ALUy ccut(inpA,inpB,inpC,opcode,outputWQ2Y,zero_flagQ2Y,neg_flagQ2Y);
14
15
16     initial begin
17         #100
18         opcode = 3'b000;
19         inpC = 1'b1;
20         inpA = 16'd7;
21         inpB = 16'd64;|
22
23         #100 inpC = 1'b0;
24         #100 opcode = 3'b001;
25         #100 opcode = 3'b010;
26         #100 opcode = 3'b011;
27         #100 opcode = 3'b100;
28         #100 opcode = 3'b101;
29         #100 opcode = 3'b110;
30         #100 opcode = 3'b111;
31         #100
32         opcode = 3'b000;
33         inpB = $random;
34         repeat(5) begin
35             #100
36             opcode = $random;
37             inpA = $random;
38         end
39         #100 $stop;
40
41     end
42 endmodule
```

Here is the timing diagram:

 

Part b:

Now we use Yosys to synthesize the code.

(Results of synthesis in Yosys without our library).

```
=== design hierarchy ===  
  
Q2_ALU                1  
  adder_op            1  
  and_op              1  
  concat_op           1  
  mux                 3  
  mux_c               1  
  not_op              1  
  or_op               1  
  shift_right_op      1  
  
Number of wires:      352  
Number of wire bits:  1004  
Number of public wires: 55  
Number of public wire bits: 707  
Number of memories:   0  
Number of memory bits: 0  
Number of processes:  0  
Number of cells:      427  
  $ _AND_             30  
  $ _AOI3_            11  
  $ _MUX_             112  
  $ _NAND_            22  
  $ _NOR_              7  
  $ _NOT_             73  
  $ _OAI3_            57  
  $ _OAI4_            48  
  $ _OR_              34  
  $ _XNOR_            16  
  $ _XOR_             17
```

Number of cells is decreased.(from 446 to 427)

Result of gates using the library provided:

```
4.2.2. Re-integrating ABC results.
ABC RESULTS:      NAND cells:      37
ABC RESULTS:      NOR cells:       110
ABC RESULTS:      NOT cells:        48
ABC RESULTS:      internal signals:  75
ABC RESULTS:      input signals:     33
ABC RESULTS:      output signals:    16
Removing temp directory.
```

Adder_op

```
4.3.2. Re-integrating ABC results.
ABC RESULTS:      NOR cells:        16
ABC RESULTS:      NOT cells:        32
ABC RESULTS:      internal signals:  0
ABC RESULTS:      input signals:     32
ABC RESULTS:      output signals:    16
Removing temp directory.
```

And_op

```
4.5.2. Re-integrating ABC results.
ABC RESULTS:      NAND cells:       81
ABC RESULTS:      NOR cells:        51
ABC RESULTS:      NOT cells:         2
ABC RESULTS:      internal signals:  69
ABC RESULTS:      input signals:     66
ABC RESULTS:      output signals:    16
Removing temp directory.
```

mux

```
4.7.2. Re-integrating ABC results.
ABC RESULTS:      NOT cells:         16
ABC RESULTS:      internal signals:  0
ABC RESULTS:      input signals:     16
ABC RESULTS:      output signals:    16
Removing temp directory.
```

Mux_c

```
4.8.2. Re-integrating ABC results.
ABC RESULTS:      NAND cells:        16
ABC RESULTS:      NOT cells:         32
ABC RESULTS:      internal signals:  0
ABC RESULTS:      input signals:     32
ABC RESULTS:      output signals:    16
Removing temp directory.
```

Not_op

```
4.1.2. Re-integrating ABC results.
ABC RESULTS:      NAND cells:        58
ABC RESULTS:      NOR cells:         5
ABC RESULTS:      NOT cells:         49
ABC RESULTS:      internal signals:  14
ABC RESULTS:      input signals:     33
ABC RESULTS:      output signals:    17
Removing temp directory.
```

Or_op

concat

```
4.4. Extracting gate netlist of module '\concat_op' to '<abc-temp-dir>/input.blif'..
Extracted 0 gates and 0 wires to a netlist network with 0 inputs and 0 outputs.
Don't call ABC as there is nothing to map.
Removing temp directory.
```

```
4.1.2. Re-integrating ABC results.
ABC RESULTS:      NAND cells:      58
ABC RESULTS:      NOR cells:       5
ABC RESULTS:      NOT cells:       49
ABC RESULTS:      internal signals: 14
ABC RESULTS:      input signals:   33
ABC RESULTS:      output signals:  17
```

Q2_ALU

```
4.9. Extracting gate netlist of module '\shift_right_op' to '<abc-temp-dir>/input.blif'.
Extracted 0 gates and 0 wires to a netlist network with 0 inputs and 0 outputs.
Don't call ABC as there is nothing to map.
Removing temp directory.
```

Shift_right_op

Number of cells: 556

Part c: It is shown above.

Part d:

Like question 1, part a is made by Verilog using software components like always and case statements, we don't know what hardware implementations does Verilog use for the statements, but yosys simulates the hardware using gates and library provided. I think is that part c is slower because it is completely made by hardware and gates and sth that are limited -> I

mean the limited gates that are in the library provided.

To calculate the time delay: we use again this command while we are in vsim. "time {run -all}"

Time for part a:

```
# Break in Module tb_ALU_2 at F:/Madar_CA/CA3/Q2_ALU_TB.v line 38  
# 230331 microseconds per iteration
```

And this is for part c:

```
# Break in Module tb_ALU_2 at F:/Madar_CA/CA3/Q2_ALU_TB.v line 38  
# 250684 microseconds per iteration
```

Question 3:

If we compare the synthesized results of question 1 and 2, we can conclude that question 2 circuit is much more efficient because of the hardware implementation and somehow use brain 😊 and some fascinating ways to minimize the circuit.

But it is hard to design these circuits and these are a little slower so there is no free lunch!