 


Q1:

Part a:





S	R	Q
0	0	invalid
0	1	1
1	0	0
1	1	Q (memory)

```

1  `timescale 1ns/1ns
2  module SRL_q1_2inp (input S, R, output Q, Qb);
3      nand #8 N1(Q, Qb, S);
4      nand #8 N2(Qb, Q, R);
5  endmodule
6
7  `timescale 1ns/1ns
8  module SRL_q1_3inp (input S, R, inp_s, inp_r, output Q, Qb);
9      nand #12 N1(Q, S, inp_s, Qb);
10     nand #12 N2(Qb, R, inp_r, Q);
11 endmodule

```

Part b:

 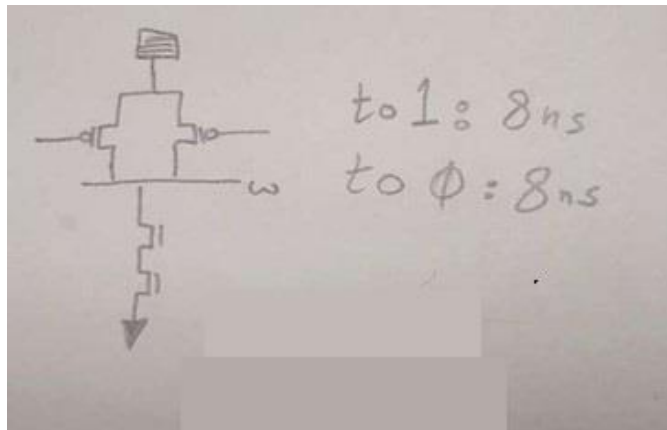


Part c:

```

F:/Madar_CA/CA4/SR_Latch_q1_tb.sv (/tbq1) - Default
Ln#
1  `timescale 1ns/1ns
2  module tbq1();
3      logic S=0,R=1;
4      wire Q, QB;
5      wire QQ, QQB;
6      SRL_q1_2inp u(S, R, Q, QB);
7      SRL_q1_3inp ut(S, R, S, R, QQ, QQB);
8
9      initial begin
10         #100 S = 0; R = 0;
11         #100 S = 1; R = 1;
12
13         #100 S = 1; R = 0;
14         #100 S = 1; R = 1;
15         #100 S = 0; R = 0;
16         #100 S = 1; R = 1;
17         #100 S = 0; R = 1;
18         #100 $stop;
19     end
20
21 endmodule
22

```

 



When S & R are simultaneously active, the loss of memory occurs. And because they are active low, when S & R are 0, that memory loss happens. When we change 00 to 11 we can see that because there are 2 ways to calculate the Q & Q complement and because of these things we see waveform changes quickly (somehow glitch occurs).


Q2:

  Part a:

```
Ln#
1  `timescale 1ns/1ns
2  module Q2_edge(input D, clk, output Q, Qb);
3      wire G1_out, G2_out, G3_out, G4_out;
4      SRL_q1_2inp G1_G2(G4_out, clk, G1_out, G2_out);
5      SRL_q1_3inp G3_G4(G2_out, D, clk, D, G3_out, G4_out);
6      SRL_q1_2inp G5_G6(G2_out, G3_out, Q, Qb);
7  endmodule
```

```
F:/Madar_CA/CA4/Q2_egde_tb.sv (/tbq2) - Default
Ln#
1  `timescale 1ns/1ns
2  module tbq2();
3      logic D = 0, clk = 0;
4      wire Q, Qb;
5      Q2_edge DFF(D, clk, Q, Qb);
6      always #100 clk = ~clk;
7      initial begin
8          repeat (15) #120 D = $random;
9          #100 $stop;
10     end
11 endmodule
12
```



 

At the positive edge of the clock, the output will get the value of D input.

(1 to 0) :

$$Q = 0$$

$$Q_{\text{bar}} = 1$$

(0 to 1):


$Q = 16$

$Q_{\text{bar}} = 24$

Part c:

Setup time is 13ns 😬


```
Ln# |  
1   | `timescale 1ns/1ns  
2   | module tbq2_c_d();  
3   |     logic D = 0, clk = 0;  
4   |     wire Q, Qb;  
5   |     Q2_edge DFF (D, clk, Q, Qb);  
6   |     always #100 clk = ~clk;  
7   |     initial begin  
8   |         #50 D = 1;  
9   |         #238 D = 0;  
10  |         #300 $stop;  
11  |     end  
12  | endmodule
```

 


Part d:

Hold time is 1ns 🤔

```
1  `timescale 1ns/1ns
2  module tbq2_c_d();
3      logic D = 0, clk = 0;
4      wire Q, Qb;
5      Q2_edge DFF (D, clk, Q, Qb);
6      always #100 clk = ~clk;
7      initial begin
8          #50 D = 0;
9          #200 D = 1;
10         #50 D = 0;
11         #300 $stop;
12     end
13 endmodule
```

 

Question 3:

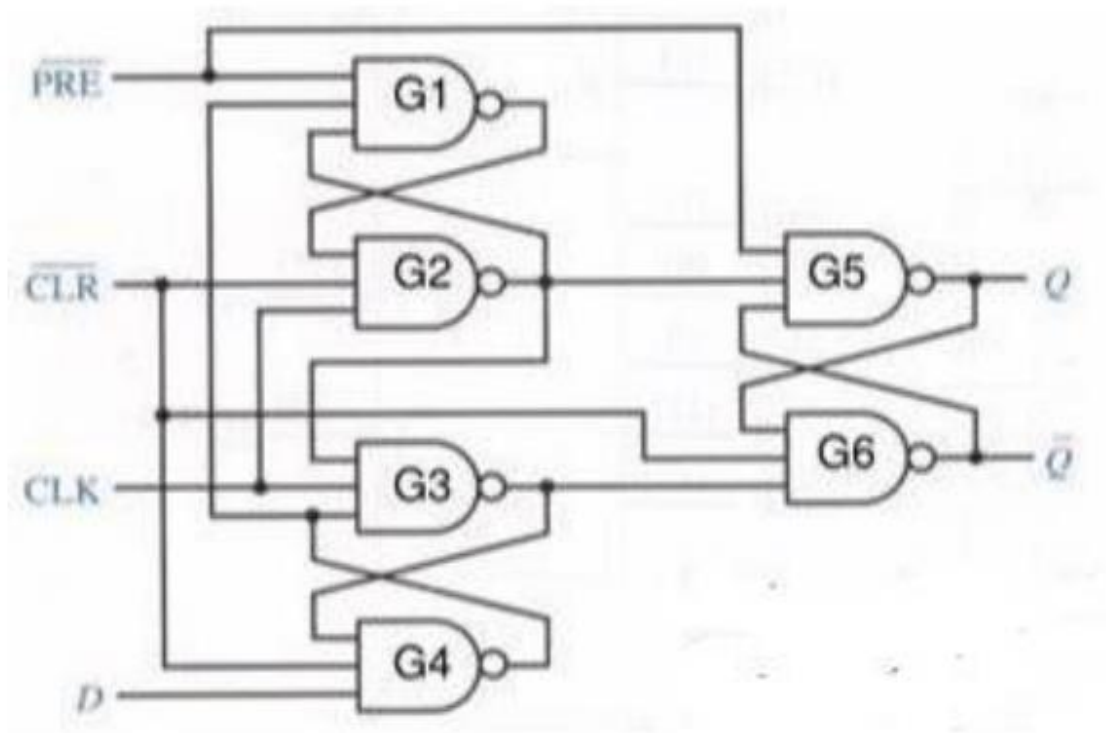


Part e:

```

Ln#
1 module Q3_pre_clr(input D, clk, pre, clr, output Q, Qb);
2     wire G1_out, G2_out, G3_out, G4_out;
3     SRL_q1_3inp G1_G2(G4_out, clk, pre, clr, G1_out, G2_out);
4     SRL_q1_3inp G3_G4(clk, D, G2_out, clr, G3_out, G4_out);
5     SRL_q1_3inp G5_G6(pre, G3_out, G2_out, clr, Q, Qb);
6 endmodule

```

Part f:

 

When D changes from 0 to 1: $\text{delay}(Q) = 24\text{ns}$ and $\text{delay}(Qb) = 36\text{ns}$

When D changes from 1 to 0: $\text{delay}(Q) = 36\text{ns}$ and $\text{delay}(Qb) = 24\text{ns}$

When Pre is active: $\text{delay}(Q) = 12\text{ns}$ and $\text{delay}(Qb) = 48\text{ns}$

When CLR is active: $\text{delay}(Q) = 24\text{ns}$ and $\text{delay}(Qb) = 12\text{ns}$

Part g:

the output retains what it was (nothing happens), because PRE and CLR are asynchronous and they are independent from clock. When we clock, if one of PRE or CLR is active, it doesn't pay attention to clock and the output changes to PRE($Q = 1$) or CLR($Q = 0$).

Part h:

$\text{PRE} \rightarrow Q = 1$

$\text{CLR} \rightarrow Q = 0$

$\text{PRE and CLR} \rightarrow Q = Q_b = 1 \rightarrow \text{memory loss occurs.}$